

```
1  // Eugene Ngo
2  // 11/18/2022
3  // EE 271
4  // Lab 4
5
6  // doubleFlip module takes in clk, reset, and button as 1-Bit inputs and returns 1-Bit out.
7  // This module processes buttons at clock cycles.
8
9  module doubleFlip (clk, reset, button, out);
10
11     input logic clk, reset;
12     input logic button;
13     output logic out;
14
15     logic out_ff1;
16
17     always_ff @(posedge clk) begin
18         out_ff1 <= button;
19     end
20
21     always_ff @(posedge clk) begin
22         out <= out_ff1;
23     end
24 endmodule
25
26 // doubleFlip_testbench tests all expected, unexpected, and edgecase behaviors
27
28 module doubleFlip_testbench();
29
30     logic clk, reset;
31     logic button;
32     logic out;
33
34     doubleFlip dut (.clk, .reset, .button, .out);
35
36     //Set up the clock
37     parameter CLOCK_PERIOD = 100;
38     initial begin
39         clk <= 0;
40         forever #(CLOCK_PERIOD / 2)
41             clk <= ~clk;
42     end
43
44     initial begin
45         reset <= 1; @ (posedge clk);
46         reset <= 0; @ (posedge clk);
47         reset <= 0; @ (posedge clk);
48         button <= 1; @ (posedge clk);
49         button <= 1; @ (posedge clk);
50         button <= 0; @ (posedge clk);
51         button <= 0; @ (posedge clk);
52         button <= 0; @ (posedge clk);
53         button <= 0; @ (posedge clk);
54         button <= 0; @ (posedge clk);
55         button <= 0; @ (posedge clk);
56         button <= 0; @ (posedge clk);
57         button <= 0; @ (posedge clk);
58         $stop;
59     end
60 endmodule
```