

```

1  // Eugene Ngo
2  // 12/2/2022
3  // EE 271
4  // Lab 5
5
6  // normalLight module takes in clk, reset, L, R, NL, NR, restart as inputs and they are all
  1-bit and returns
7  // lightOn which is also 1-bit. This module determines the next state based on the inputs
  and moves the light
8  // to the left if key 3 is pressed and moves the light to the right if key 0 is pressed.
  When the game is reset
9  // these lights are turned off.
10
11 module normalLight(lightOn, clk, reset, L, R, NL, NR, restart);
12
13     output logic lightOn;
14     input logic clk, reset;
15     input logic L, R, NL, NR, restart;
16
17     enum {on, off} ps, ns;
18
19     always_comb begin
20         case(ps)
21             on:      if(~R & L | R & ~L) ns = off;
22                     else ns = on;
23
24             off:     if(NR & L & ~R | NL & R & ~L) ns = on;
25                     else ns = off;
26
27         endcase
28     end
29
30     always_comb begin
31         case(ps)
32             on: lightOn = 1;
33
34             off: lightOn = 0;
35
36         endcase
37     end
38
39     always_ff @(posedge clk) begin
40         if(reset | restart)
41             ps <= off;
42         else
43             ps <= ns;
44     end
45 endmodule
46
47 // normalLight_testbench tests all expected, unexpected, and edgecase behaviors
48 module normalLight_testbench();
49     logic L, R, NL, NR;
50     logic lightOn;
51     logic clk, reset;
52
53     normalLight dut (.lightOn, .clk, .reset, .L, .R, .NL, .NR);
54
55     //Set up the clock
56     parameter CLOCK_PERIOD = 100;
57     initial begin
58         clk <= 0;
59         forever #(CLOCK_PERIOD / 2)
60             clk <= ~clk;
61     end
62
63     // Each line is one clock cycle
64     initial begin
65
66         reset <= 1;
67
68         reset <= 0;
69
70         L <= 1; R <= 0; NL <= 0; NR <= 1;

```

```
71      @(posedge clk);
72      @(posedge clk);
73      @(posedge clk);
74      NL <= 1; NR <= 0;
75      @(posedge clk);
76      @(posedge clk);
77      @(posedge clk);
78      L <= 0; R <= 1;
79      @(posedge clk);
80      @(posedge clk);
81      @(posedge clk);
82      NL <= 0; NR <= 1;
83      @(posedge clk);
84      @(posedge clk);
85      @(posedge clk);
86      L <= 1;      NL <= 1; NR <= 0;
87      @(posedge clk);
88      @(posedge clk);
89      @(posedge clk);
90      reset <= 1;
91      @(posedge clk);
92      @(posedge clk);
93      L <= 0; R <= 1; NL <= 1; NR <= 0;
94      @(posedge clk);
95      @(posedge clk);
96      L <= 1; R <= 0; NL <= 0; NR <= 0;
97      @(posedge clk);
98      @(posedge clk);
99      L <= 0; R <= 1; NL <= 0; NR <= 0;
100     @(posedge clk);
101     @(posedge clk);
102     $stop;
103     end
104 endmodule
```